

Keywords: pushbutton power switches, switch debouncers, LDO linear regulator, flip-flops

## APPLICATION NOTE 4444

# Single-Pushbutton ON/OFF Power Control

By: Tina Alikahi  
 Sep 11, 2009

*Abstract: This application note presents a single-pushbutton power-control circuit. The design consists of an ON/OFF control circuit comprised of a pushbutton, debouncer, and flip-flop. This circuit toggles the power output voltage by controlling an LDO. The design features the MAX6816 debouncer and MAX6484 LDO.*

This design idea appeared in the October 30, 2006 issue of *Portable Design* magazine.

The design of a handheld device today requires that you simplify and reduce the controls to a minimum. A circuit that enables a single pushbutton to turn power on and off can be very useful. **Figure 1** shows a single-pushbutton power-control circuit that consists of only a few small components, and consumes little power.

The normally open (NO) single-contact pushbutton connects to a debouncer (the [MAX6816](#), IC1) that guarantees a single-output edge (rise or fall) each time the button is pushed or released. The MAX6816's output drives the clock input of a flip-flop (IC2) wired as a T-type (toggle) flip-flop. The flip-flop output, in turn, controls a low-dropout (LDO) linear regulator (the [MAX6484](#), IC3). The MAX6484 powers a handheld gadget, which turns on or off each time that the pushbutton is operated. The same circuit can also drive other types of power regulator, if the regulator features a logic-level power-management input.

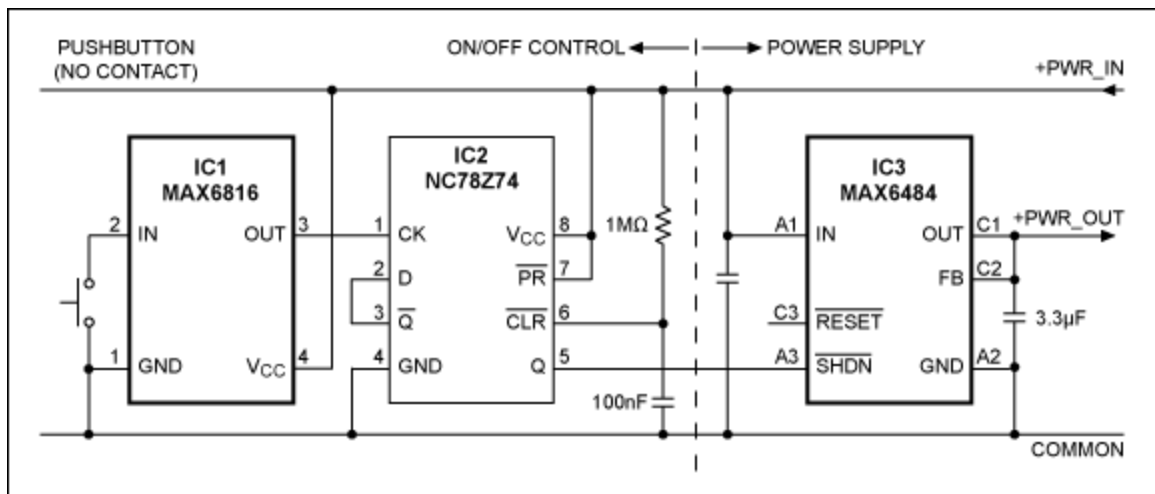


Figure 1. This normally open pushbutton connects to a debouncer, the MAX6816 (IC1) and IC2. This single-pushbutton ON/OFF control circuit lets you toggle the PWR OUT voltage by controlling the MAX6484 LDO (IC3).

The 1M $\Omega$  resistor and 100nF capacitor connected to the flip-flop's CLR input ensure that the circuit always powers up in the same state (OFF) when PWR\_IN is connected first. The ON/OFF control circuit (pushbutton, debouncer, and flip-flop) operates between 2V and 5.5V; it draws about 3.5 $\mu$ A when the supply voltage is 3.5V. The MAX6816 is available in a 4-pin SOT143 package, IC2 in an MO-187 package, and the MAX6484 in a 6-ball UCSP™ package.

UCSP is a trademark of Maxim Integrated Products, Inc.

#### Related Parts

<a href="#">MAX6484</a>	300mA LDO Linear Regulators with Internal Microprocessor Reset Circuit	
<a href="#">MAX6816</a>	$\pm$ 15kV ESD-Protected, Single/Dual/Octal, CMOS Switch Debouncers	<a href="#">Free Samples</a>

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 4444: <http://www.maximintegrated.com/an4444>

APPLICATION NOTE 4444, AN4444, AN 4444, APP4444, Appnote4444, Appnote 4444

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>